

School of Electronics and Computing Systems
20-ECEE-352

ELECTRONICS II
Spring Quarter 2010

Homework #2.
Due: Wednesday April 14, 2010

Problem 1: An amplifier has a gain transfer function

$$A(s) = 10 \frac{s}{(s + 2\pi \times 10)} \frac{1}{\left(1 + \frac{s}{2\pi \times 10^6}\right)}$$

Sketch a Bode plot for its magnitude and find the mid-band gain, lower 3-dB f_L , and upper 3-dB frequency F_H . Also, find the approximate values for the frequencies at which the gain becomes unity.

Problem 2. If in the circuit below, A is an ideal voltage amplifier of gain 100, find A_M , $F_L(s)$, and $F_H(s)$. Also, find ω_L and ω_H .

