

Department
of
Electrical and Computer Engineering, UC.
EE - 352
ELECTRONICS II
SUMMER QUARTER 2010

HOMEWORK ASSIGNMENT #4
Due April 30, 2010

Problem P10.71

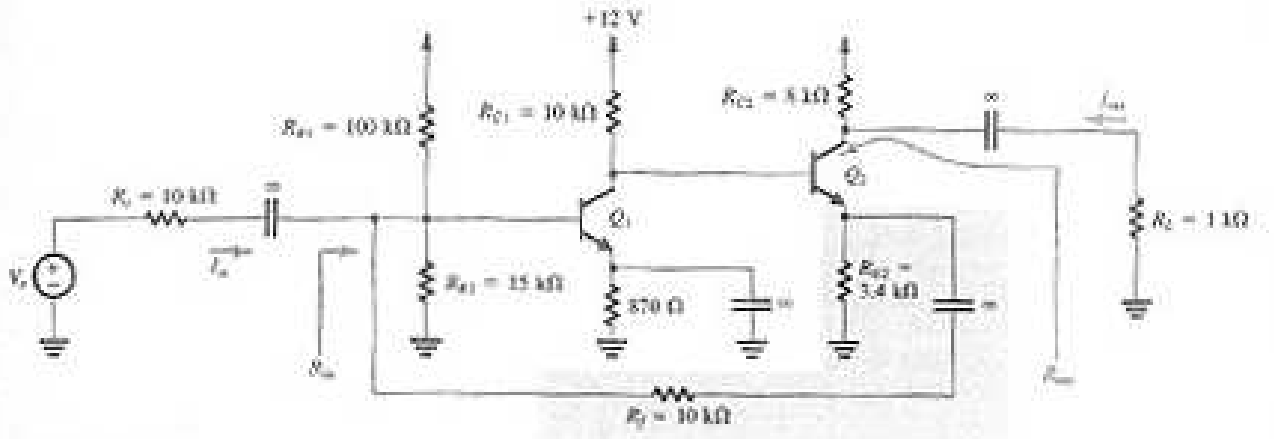


Figure P10.71

Figure P10.71 shows a feedback amplifier utilizing the shunt-series topology. All transistors have $\beta=100$ and $V_{BE}=0.7V$.

- (a) Perform a dc analysis to find the emitter currents in Q_1 and Q_2 and hence determine their small signal parameters.
- (b) Replacing the BJTs with their hybrid π models, give the equivalent circuit of the feedback amplifier circuit
- (c) Give the A circuit and determine A , R_i and R_o . Note that R_o is the resistance determined by breaking the emitter loop of Q_2 and measuring the resistance between the terminals thus created.
- (d) Find β circuit and determine the value of β .
- (e) Find $A\beta$, $1+A\beta$, A_f , R_{of} , R_{if} . Note that R_{of} represents the resistance that in effect appears in the center of Q_2 as a result of feedback.