ECE-611 Microwave Communications Terminated Transmission Lines

Basic difference between lumped elements and distributed circuit elements is the frequency response of a given circuit.

For example, when a series LC network is considered (neglecting the losses), the input impedance is written as



 $Z_{in}=j\omega L+1/j\omega C$

The frequency response of the input impedance for the series LC network is plotted in the figure above. Here the impedance is imaginary all the time, it is infinity at $\omega=0$, is capacitive up to a frequency $\omega=1/(LC)^{1/2}$ and becomes positive (inductive) above that is frequency and approaches $j\infty$ as the frequency increases. Thus, the impedance goes through zero once. Lumped parameters exhibit a different response as will be shown below.

Transmission Lines

On a transmission line, the total Voltage and Current at z are

$$V(z) = V^{+} e^{-j\beta z} + V^{-} e^{+j\beta z}$$

$$I(z) = I^{+} e^{-j\beta z} + I^{-} e^{+j\beta z}$$

$$I(z) = \frac{1}{Z_{c}} [V^{+} e^{-j\beta z} - V^{-} e^{+j\beta z}]$$

A load Z_L is connected at the output terminals of the transmission line. By definition, the Load Impedance is

$$Z_{L} = \frac{V(0)}{I(0)}$$
$$Z_{L} = \frac{V^{+} + V^{-}}{\frac{1}{Z_{c}}(V^{+} - V^{-})} = Z_{c} \frac{1 + \frac{V^{-}}{V^{+}}}{1 - \frac{V^{-}}{V^{+}}}$$

Define Reflection coefficient (complex quantity) as

$$\Gamma_{L} = \frac{V^{-}(0)}{V^{+}(0)} = \frac{V^{-}}{V^{+}} = \rho_{L} e^{j\theta}$$
$$Z_{L} = Z_{c} \frac{1 + \Gamma_{L}}{1 - \Gamma_{L}}$$

Solving for $\,\Gamma_{L}\,,$ we obtain

$$\Gamma_{\rm L} = \frac{Z_{\rm L} - Z_{\rm c}}{Z_{\rm L} + Z_{\rm c}}$$

Reflection coefficient at any length z=-d is

$$\Gamma(z = -d) = \frac{V^{-}(d)}{V^{+}(d)} = \frac{V^{-} e^{-j\beta d}}{V^{+} e^{+j\beta d}} = \Gamma_{L} e^{-j2\beta d} = \rho_{L} e^{j\theta} e^{-j2\beta d} = \rho_{L} e^{j(\theta - 2\beta d)}$$

Magnitude is determined by the load reflection coefficient and does not change but phase changes

By definition, the input Impedance at z=-d is

$$Z_{in}(z=-d) = \frac{V(z=-d)}{I(z=-d)}$$

$$Z_{in} = \frac{V^{+}e^{+j\beta d} + V^{-}e^{-j\beta d}}{\frac{1}{Z_{c}}(V^{+}e^{+j\beta d} - V^{-}e^{-j\beta d})} = Z_{c} \frac{1 + \frac{V^{-}}{V^{+}}e^{-j2\beta d}}{1 - \frac{V^{-}}{V^{+}}e^{-j2\beta d}} = Z_{c} \frac{1 + \Gamma_{L}e^{-j2\beta d}}{1 - \Gamma_{L}e^{-j2\beta d}}$$

Manipulating the equation, \mathbf{Z}_{in} is simplified to

$$Z_{in} = Z_c \frac{Z_L + j Z_c \tan(\beta d)}{Z_c + j Z_L \tan(\beta d)}$$

In terms of Admittance parameters,

$$Y_{in} = Y_c \frac{Y_L + jY_c \tan(\beta d)}{Y_c + jY_L \tan(\beta d)}$$

Various load conditions

$$Z_{L} = Z_{c} \quad (\text{matched load})$$

$$\Gamma_{L} = \frac{Z_{c} - Z_{c}}{Z_{c} + Z_{c}} = 0, \quad \Gamma(z = -d) = \Gamma_{L} e^{-j2\beta d} = 0$$

$$Z_{in} = Z_{c} \frac{Z_{c} + j Z_{c} \tan(\beta d)}{Z_{c} + j Z_{c} \tan(\beta d)} = Z_{c}$$

$$Z_{L} = 0 \implies \text{short circuit}$$

$$\Gamma_{L} = \frac{0 - Z_{c}}{0 + Z_{c}} = -1$$

$$Z_{in} = Z_{c} \frac{0 + j Z_{c} \tan(\beta d)}{Z_{c} + j 0 \tan(\beta d)} = j Z_{c} \tan(\beta d)$$



The impedance repeats itself every $\lambda/2$.

$$d = \frac{\lambda}{4} \rightarrow \beta d = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \quad (\text{quarter-wavelength})$$

$$\Gamma(-d) = \Gamma_L e^{-j2\beta d} = \Gamma_L e^{-j\pi} = -\Gamma_L$$

$$Z_{\text{in}} = Z_c \frac{Z_L + j Z_c \tan\left(\frac{\pi}{2}\right)}{Z_c + j Z_L \tan\left(\frac{\pi}{2}\right)} = Z_c \frac{Z_L + j Z_c \infty}{Z_c + j Z_L \infty} = Z_c \frac{Z_c}{Z_L} = \frac{Z_c^2}{Z_L} \quad \left[\text{ since } \tan\left(\frac{\pi}{2}\right) = \infty\right]$$

The impedance is inverted. Short circuit becomes an open circuit and an open circuit becomes a short circuit if the line length is quarter wavelength.

As can be seen from these results that the impedance of a transmission line with an arbitrary load repeats itself every $\lambda/2$.