## EE-611 Microwave Communications Supplementary Notes. Network Representation of Microwave Systems

## **S**-Parameters

It is difficult or impossible to measure true voltages and currents at a given port. Therefore, impedance and admittance matrix concepts are not useful at microwave frequencies. In place of this, one can relate the incident voltages to reflected voltages at the ports. This results in a realizable and measurable characterization of the microwave circuits. In the N-port microwave system shown below, at each port and at the specified reference terminal plane,  $V_n^+$ , the incident and  $V_n^-$ , reflected wave are given. Each port has a characteristic impedance of  $Z_n^-$  ohms.



S-parameters are defined by

$V^{-}_{1}$		$S_{11}$	$S_{12}$	•	•	•	$S_{1N}$	$V^{+}_{1}$
$V_2^-$		$S_{21}$	<i>S</i> <sub>22</sub>		•	•	$S_{2N}$	$V_2^+$
•	=	•	•	•	•	•	•	•
•		•	•	•	•	•	•	•
•		•	•	•	•	•	•	
$V^{-}{}_{N}$		$S_{N1}$	$S_{N2}$				$S_{_{NN}}$	$V^{+}{}_{N}$

Various S-parameters can be found from

$$S_{ii} = \frac{V_i}{V_i^+} \Big|_{all} V_{n\neq i}^+ = 0$$

i.e., all ports are matched to their characteristic impedance: all the reflected voltages are zero.  $S_{ii}$  in nothing else than the reflection coefficient of the port *i* at the terminal plane  $t_i$ .

Similarly,

$$S_{ij} = \frac{V_i^-}{V_j^+} \quad \text{all } V_{n-j}^+ = C$$

This in nothing else than the transmission coefficient from port *j* to port *i* when all *n* ports (except n=j) are matched to their characteristic impedance.

## **Properties of S-Parameters**

S parameter equation can be written in terms of matrices as

 $[V^{-}] = [S][V^{+}]$ 

Here [S] matrix is given by

	$S_{11}$	$S_{12}$		•			$S_{1N}$
	S <sub>21</sub>	S <sub>22</sub>			•		$S_{2N}$
	•	•	•	•	•	•	•
[S] =	•	•	•	•	•	•	•
	•	•	•	•	•	•	•
	•	•	•	•	•	•	•
	$S_{N1}$	$S_{N2}$					S <sub>NN</sub>

## **Properties**

• If the reference terminal planes are shifted toward outside by an electrical length l, then the new [S'] matrix is given by

S <sup>'</sup> =		$e^{-j} \ _1 l_1$	0	0		 0	$S_{11}$	$S_{12}$	•	•		•	$S_{1N} \\$	$e^{-j} \ {}_1^{l_1}$	0	0		0
		0	$e^{-j} \ _2 l_2$	0	•	 0	S <sub>21</sub>	S <sub>22</sub>	•	•			$S_{2N}$	0	$e^{-j_{2}l_{2}}$	0		0
		0	0	$e^{-j} \ _3 l_3$		 0	•	•	•	•			•	0	0	$e^{-j_{3}l_{3}}$		0
	=					 0	•	·	•	•	•	•	•					0
						 0	•	•	•	•	•	•	•					0
						 0	•	•	•	•	•	•	•					0
		0	0	0		 $e^{-j} N^{l} N$	$S_{N1}$	$S_{N2}$					$S_{NN}$	0	0	0		e <sup>-j</sup> N <sup>l</sup> N

• If normalized voltages are used, the scattering matrix is symmetric, i.e.,  $S_{nm}=S_{mn}$ . In matrix form this can be written as

$$[S] = [S]_t$$

• For a lossless network,

$$N = N$$

$$|S_{ni}| = N$$

$$S_{ni}S_{ni}^{*} = 1$$

$$N$$

$$S_{ns}S_{nr}^{*} = 0$$

$$S_{nr}$$

This implies that [S] is unitary, i.e.,

$$[S]^* = [S]_t^{-1}$$

• Normalized voltages are defined as

$$b_{1} = \frac{V_{1}^{-}}{\sqrt{Z_{1}}} \qquad b_{2} = \frac{V_{2}^{-}}{\sqrt{Z_{2}}} \qquad \dots \qquad b_{n} = \frac{V_{n}^{-}}{\sqrt{Z_{n}}}$$
$$a_{1} = \frac{V_{1}^{+}}{\sqrt{Z_{1}}} \qquad a_{2} = \frac{V_{2}^{+}}{\sqrt{Z_{2}}} \qquad \dots \qquad a_{n} = \frac{V_{n}^{+}}{\sqrt{Z_{n}}}$$

• For a lossless network the total power is conserved. That is the incident power is equal to the reflected power

$$N = N \\ |b_i|^2 = |a_i|^2 \\ i=1 = n=1$$

• The generalized scattering parameters are then defined in terms of the normalized voltages (as an example for a two port network)

- The relation between the unnormalized and generalized (normalized) S parameters can be written as (as an example  $S_{\rm 12})$ 

$$\mathbf{S}_{12}^{'} = \frac{\mathbf{b}_{1}}{\mathbf{a}_{2}} = \frac{\mathbf{v}_{1}^{-}}{\frac{\mathbf{v}_{2}^{+}}{\sqrt{Z_{1}}}} = \frac{\sqrt{Z_{2}}}{\sqrt{Z_{1}}} \mathbf{S}_{12} = \sqrt{\frac{Y_{1}}{Y_{2}}} \mathbf{S}_{12}$$

Note that  $S_{12}$  is equal to  $S_{12}$ ' if the port impedances are the same.