

15-Phys-202
S 2002

Prof. F. Mansouri
Quiz 5

Name _____

1. In the Figure the battery has the potential difference of 8.0 V. The capacitance of each of the capacitors is $2.0 \mu\text{F}$,

$$C_1 = C_2 = C_3 = C_4 = C_5 = 2.0 \mu\text{F}$$

Find

- (a) The equivalent capacitance of all the capacitors;
- (b) The charge stored on that equivalent capacitance;
- (c) Find the charge and potential on each of the capacitors.

Solution

- (a) $C_{eq} = 1.0 \mu\text{F}$;
- (b) $q = 8.0 \text{ C}$;
- (c) $V_1 = V_2 = V_4 = V_5 = 2.0 \text{ V}$, $V_3 = 4.0 \text{ V}$;
 $q_1 = q_2 = q_4 = q_5 = 4.0 \text{ C}$, $q_3 = 8 \text{ C}$;

